

数电实验7报告

17341015 数据科学与计算机学院
计科一班 陈鸿峥

1 内容一

1.1 实验目的

验证四位双向移位寄存器74LS194的功能

1.2 实验原理

\overline{Cr}	S_1	S_0	功能
0	X	X	置零
1	0	0	保持
1	0	1	右移
1	1	0	左移
1	1	1	并行送数

1.3 实验细节

1.3.1 实验仪器及器件

1. 数字电路实验箱、示波器、导线若干
2. 74LS194*1, 74LS197*1

1.3.2 实验流程


1. 将74LS197连接成十六进制作为电路的输入信号源： $\overline{PL}, \overline{MR}$ 接高电平，CP0接时钟输入
2. 将74LS194与74LS197相连，观察输出波形

1.4 结果分析及结论

静态测试：接01显示器显示正常

动态测试：实验箱连线如下

波形图如下

 

从图中可以明显看出分频特性，符合预期

2 内容二

2.1 实验目的

实现四节拍脉冲发生器

2.2 实验原理

将四位双向移位寄存器与JK触发器相连可实现效果，需要注意输入与输出不要连反，实验过程中因为逻辑门的输入输出连反，导致只有两位循环

2.3 实验细节

2.3.1 实验仪器及器件

1. 数字电路实验箱、示波器、导线若干
2. 74LS194*1, 74LS73*1, 74LS197*1


2.3.2 实验流程

1. 将74LS197连接成十六进制作为电路的输入信号源： $\overline{PL}, \overline{MR}$ 接高电平，CP0接时钟输入
2. 将74LS73与74LS194相连，按照书上连线方法将其余导线连接
3. 用示波器观测并记录波形

2.4 结果分析及结论

静态测试：接01显示器显示正常

动态测试：波形图如下

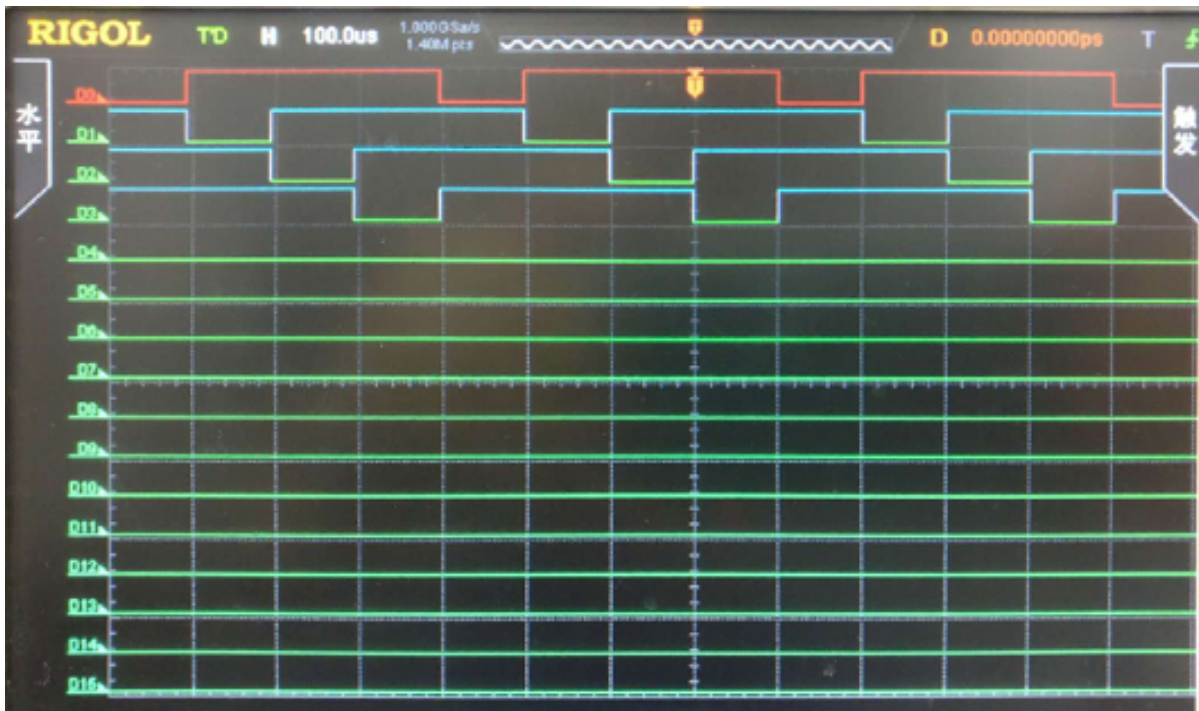

3 内容三

3.1 实验目的

实现扫描译码显示电路

3.2 实验原理

通过拨码开关来实现BCD码的输入，并将其传入到译码器中，再将译码器与七段数码管相连. 通过人眼视觉的暂存效应，当时钟频率足够快时，即可正常在数码管上显示数码.

3.3 实验细节

3.3.1 实验仪器及器件

1. 数字电路实验箱、示波器、导线若干
2. 74LS197*1
3. 74LS48*1, 74LS138*1

3.3.2 实验流程

1. 将74LS197连接成十六进制作作为电路的输入信号源： $\overline{PL}, \overline{MR}$ 接高电平，CP0接时钟输入
2. 将74LS197的输出与74LS138相连，74LS138的输出与七段数码管的选通位相连
3. 74LS48与四个拨码开关相连，输出直接与七段数码管相连

3.4 结果分析及结论

静态测试：接01显示器显示正常

动态测试：结果上课时已交给助教检查，没有存图，但可以做到通过拨码开关改变数码管的输出，且四位输出相同

4 内容四

4.1 实验目的


用LED数码管显示8位学号

4.2 实验原理

由于我的学号都是在0到7之间，所以只需接通一个74LS197的八进制计数器。

将其输出分别接到74LS48和74LS138，通过选通再加以高频时钟，即可正常实现学号的显示。

4.3 Protues仿真结果

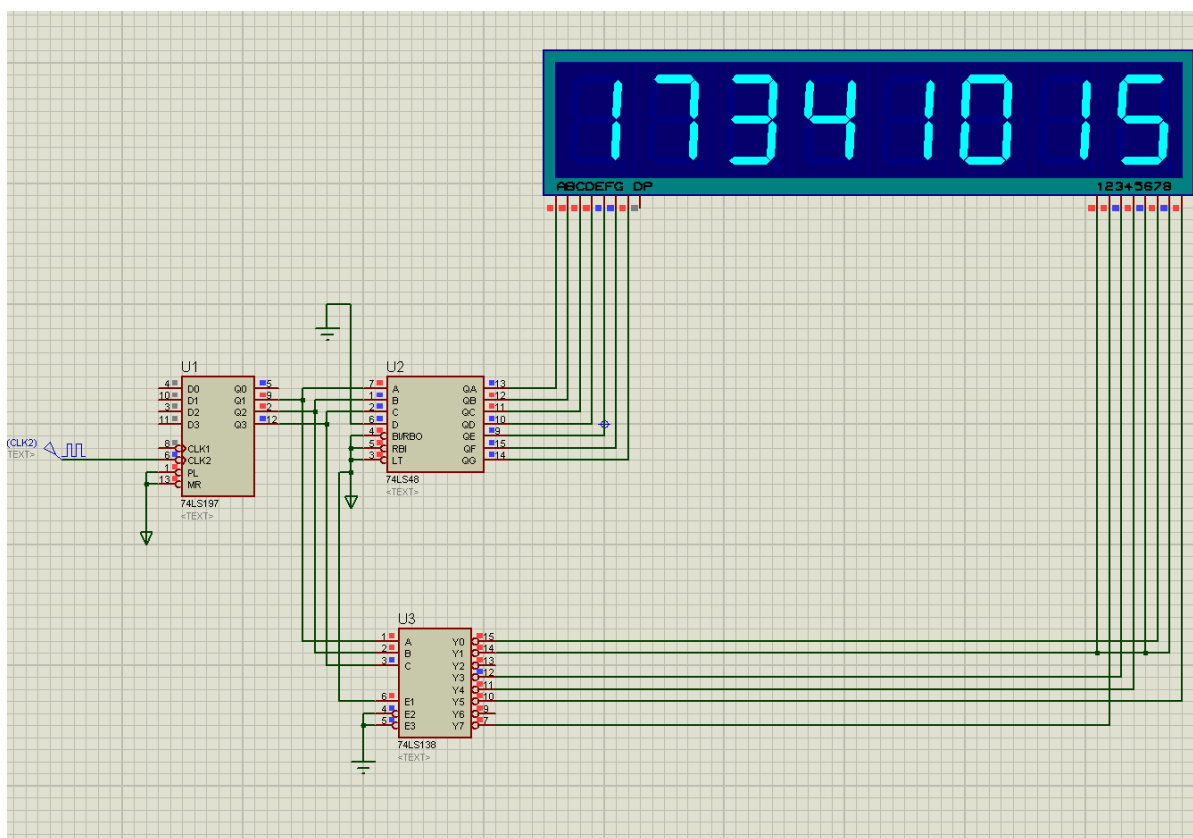

5 内容五

5.1 实验目的

在点阵面板显示图案

5.2 实验原理


点阵的行为高电平，点阵的列为低电平时，对应的点将会亮灯，故可以通过在不同的时间（行）选通不同的列来实现点阵的显示，如数字0的真值表如下

				1	2	3	4	5	6	7	8
0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	1	1	1	0	0
0	1	0	0	0	0	1	0	0	1	0	0
0	1	1	0	0	0	1	0	0	1	0	0
1	0	0	0	0	0	1	0	0	1	0	0
1	0	1	0	0	0	1	0	0	1	0	0
1	1	0	0	0	0	1	1	1	1	0	0
1	1	1	0	0	0	0	0	0	0	0	0


5.3 实验结果

数字与英文在课堂上已交由助教检查，没有存图

数字是一个0字，英文是一个H，下图是数字0的连接电路

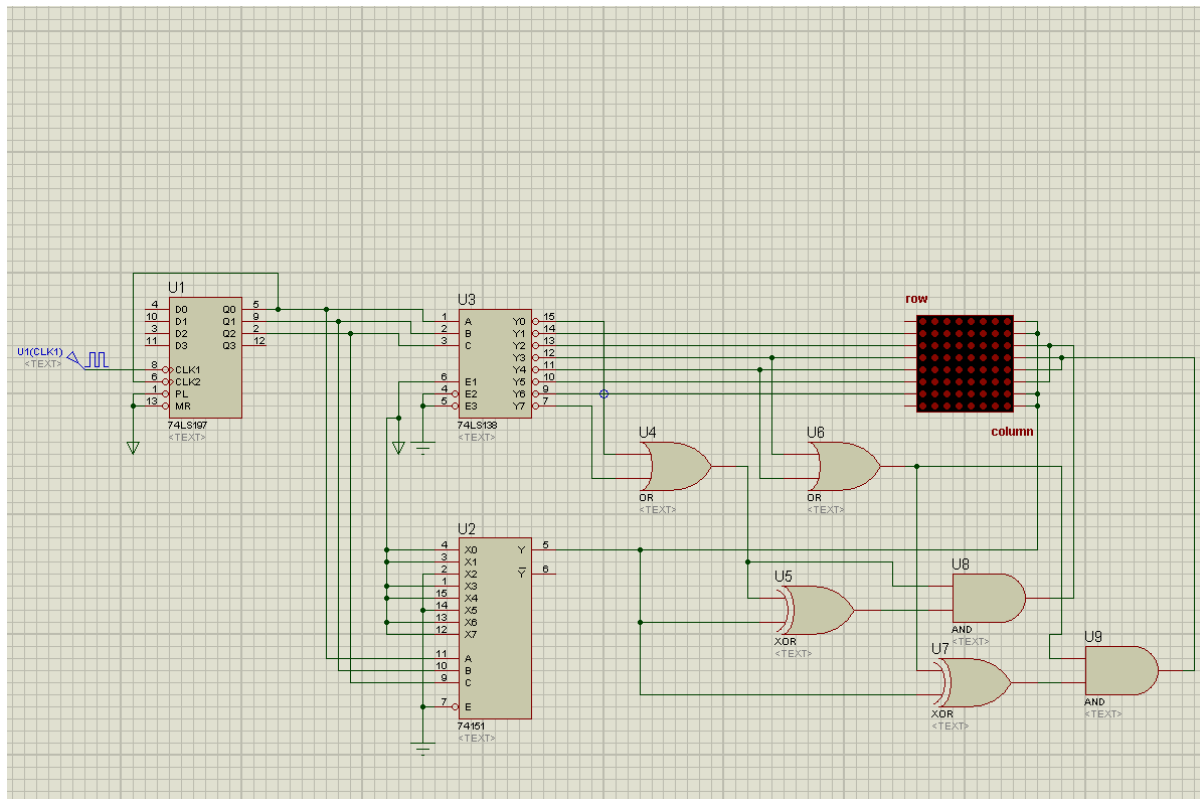

下图是一个旧字

 

6 内容六(加分题)

6.1 实验目的

在Basys3实验板上通过拨码开关，分别显示学号的前四位和后四位

6.2 Bayse板电路实现

Verilog程序如下，学号显示部分

```
module display (
    input [1:0] digit ,
    input fb ,
    output reg [6:0] seven_seg
);

// seven segments
parameter zero = 7'b000_0001;
parameter one = 7'b100_1111;
parameter two = 7'b001_0010;
parameter three = 7'b000_0110;
parameter four = 7'b100_1100;
```

```

parameter five   = 7'b010_0100;
parameter six    = 7'b010_0000;
parameter seven  = 7'b000_1111;
parameter eight  = 7'b000_0000;
parameter nine   = 7'b000_0100;

```

```

always @(digit)
if (fb == 1)
begin
    case(digit)
        0: seven_seg = four;
        1: seven_seg = three;
        2: seven_seg = seven;
        3: seven_seg = one;
    endcase // clk
end
else begin
case(digit)
    0: seven_seg = five;
    1: seven_seg = one;
    2: seven_seg = zero;
    3: seven_seg = one;
endcase // clk
end

```

endmodule

分频计数器与七段数码管连接部分

```

module Counter(
    input clr, // clear, say reset
    input wire clk, // clock
    input wire fb, // front or back
    output [6:0] seg,
    output reg [3:0] an
);

reg [1:0] out;
parameter MAXCOUNT = 4;

// time counter
localparam MAXCOUNT_TIME = 100_000; // 10kHz
reg [16:0] count; // 26 bits to store count: 2^17 > 10^5
always @ (posedge clk or posedge clr)
begin

```



```

    if (clr == 1) // reset
        count <= 0;
    else if (count == MAX_COUNT_TIME - 1) // return 0
        count <= 0;
    else
        count <= count + 1;
end

// frequency divisor (flip-flop)
reg clk_div;
always @ (posedge clk, posedge clr)
begin
    if (clr == 1)
        clk_div <= 0;
    else if (count == MAX_COUNT - 1) // reset
        clk_div <= ~clk_div;
    else // set
        clk_div <= clk_div;
end

always @ (posedge clk_div or posedge clr)
begin
    if (clr == 1)
        out <= 0;
    if (out == MAX_COUNT)
        out <= 0;
    else
        out <= out + 1;
end

display disp1 (.digit(out), .seven_seg(seg), .fb(fb));

always @ (out)
    case(out)
        0: an = 4'b1110;
        1: an = 4'b1101;
        2: an = 4'b1011;
        3: an = 4'b0111;
    endcase
endmodule

```

限制文件如下

```
set_property PACKAGE_PIN W4 [get_ports {an[3]}]
```

```



set_property PACKAGE_PIN V4 [get_ports {an[2]}]
set_property PACKAGE_PIN U4 [get_ports {an[1]}]
set_property PACKAGE_PIN U2 [get_ports {an[0]}]
set_property PACKAGE_PIN W7 [get_ports {seg[6]}]
set_property PACKAGE_PIN W6 [get_ports {seg[5]}]
set_property PACKAGE_PIN U8 [get_ports {seg[4]}]
set_property PACKAGE_PIN V8 [get_ports {seg[3]}]
set_property PACKAGE_PIN U5 [get_ports {seg[2]}]
set_property PACKAGE_PIN V5 [get_ports {seg[1]}]
set_property PACKAGE_PIN U7 [get_ports {seg[0]}]

set_property PACKAGE_PIN W5 [get_ports clk]
set_property IOSTANDARD LVCMOS33 [get_ports {an[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {an[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {an[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {an[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports clk]

set_property PACKAGE_PIN V17 [get_ports clr]
set_property PACKAGE_PIN R2 [get_ports fb]
set_property IOSTANDARD LVCMOS33 [get_ports clr]
set_property IOSTANDARD LVCMOS33 [get_ports fb]

```

最终结果图如下

  

7 心得体会

1. 学会了移位寄存器及JK触发器的使用及其功能
2. 明白译码显示电路的原理，并将其实际运用起来
3. 更好地学会用Verilog进行电路设计分析，并成功上板实现