

数电实验9报告

17341015 数据科学与计算机学院
计科一班 陈鸿峥

1 内容一

1.1 实验目的

设计16进制异步加法计数器

1.2 实验原理

1. 真值表如下

Q3	Q2	Q1	Q0	Q3	Q2	Q1	Q0
0	0	0	0	1	0	0	0
0	0	0	1	1	0	0	1
0	0	1	0	1	0	1	0
0	0	1	1	1	0	1	1
0	1	0	0	1	1	0	0
0	1	0	1	1	1	0	1
0	1	1	0	1	1	1	0
0	1	1	1	1	1	1	1

2. 次态卡诺图

		Q ₁ Q ₀			
		00	01	11	10
Q ₃ Q ₂	00	0001	0010	0100	0011
	01	0101	0110	1000	0111
	11	1101	1110	0000	1111
	10	1001	1010	1100	1011

3. 状态方程

$$Q_3^{n+1} = Q_3 \overline{Q_2} + Q_3 \overline{Q_1} + Q_3 \overline{Q_0} + \overline{Q_3} Q_2 Q_1 Q_0$$

$$Q_2^{n+1} = Q_2 \overline{Q_1} + Q_2 \overline{Q_0} + \overline{Q_2} Q_1 Q_0$$

$$Q_1^{n+1} = \overline{Q_1} Q_0 + Q_1 \overline{Q_0}$$

$$Q_0^{n+1} = \overline{Q_0}$$

4. 驱动方程，将状态方程化为JK触发器形式可得

$$J_0 = 1 \quad K_0 = 1$$

$$J_1 = Q_0 \quad K_0 = Q_0$$


$$J_2 = Q_1 Q_0 \quad K_2 = Q_1 Q_0$$

$$J_3 = Q_2 Q_1 Q_0 \quad K_3 = Q_2 Q_1 Q_0$$



1.3 实验细节

1.3.1 Protues仿真

电路图如下所示

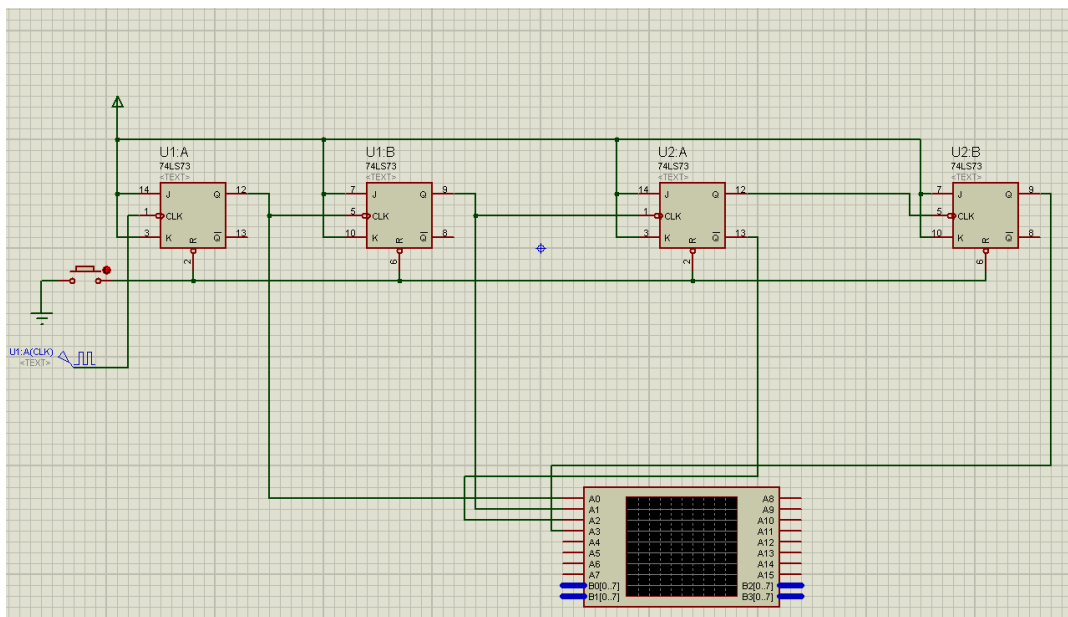

仿真结果如下

  

2 内容二

2.1 实验目的

实现16进制同步加法计数器


2.2 实验原理

同实验1


2.3 实验细节

2.3.1 Protues仿真

电路图如下所示

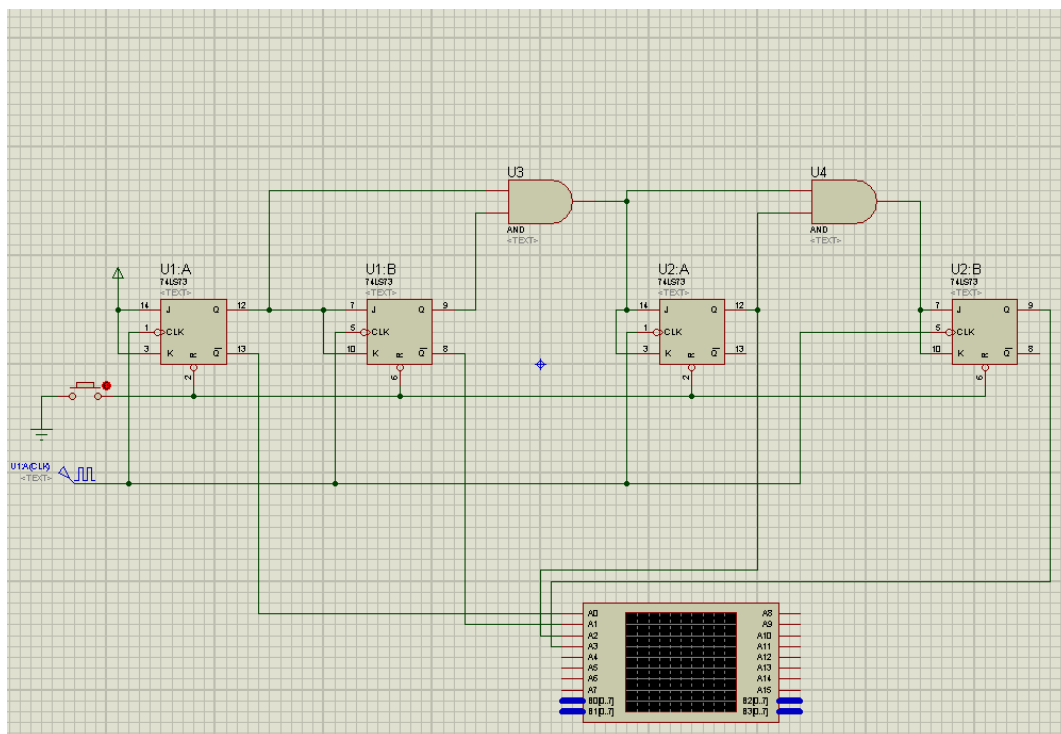

仿真结果如下

 


2.3.2 实验仪器及器件

1. 数字电路实验箱、示波器、导线若干
2. 74LS73*4

2.3.3 实验流程及结果分析

如Protues电路连线

实验箱连线如下

 

通过观察01显示器，符合波形

3 内容三

3.1 实验目的

使用JK触发器和门电路设计实现一个二进制四位计数器模仿74LS194功能

3.2 实验原理

74LS194功能如下

\overline{Cr}	S_1	S_0	功能
0	X	X	置零
1	0	0	保持
1	0	1	右移
1	1	0	左移
1	1	1	并行送数

仅左移右移次态卡诺图

Q_1Q_0D									
		000	001	011	010	110	111	101	100
Q_3Q_2	00	00010	10001	X	00110	01110	X	X	X
	01	X	X	X	X	11110	X	X	X
	11	X	11101	X	X	X	X	11111	X
	10	X	11001	X	X	X	X	X	X

状态方程

$$Q_3^{n+1} = Q_2 + D$$

$$Q_2^{n+1} = Q_3 + Q_1$$

$$Q_1^{n+1} = Q_2 + Q_1 + Q_0$$

$$Q_0^{n+1} = Q_1 + \overline{D}$$

驱动方程，将状态方程化为JK触发器形式可得

$$J_0 = \overline{\overline{Q_1} D} \quad K_0 = \overline{Q_1} D$$

$$J_1 = \overline{\overline{Q_2} \overline{Q_0}} \quad K_0 = 0$$


$$J_2 = \overline{\overline{Q_3} \overline{Q_1}} \quad K_2 = \overline{Q_3} \overline{Q_1}$$

$$J_3 = \overline{\overline{Q_2} \overline{D}} \quad K_3 = \overline{Q_2} \overline{D}$$

3.3 实验细节


3.3.1 Protues仿真

全功能74LS194电路图如下

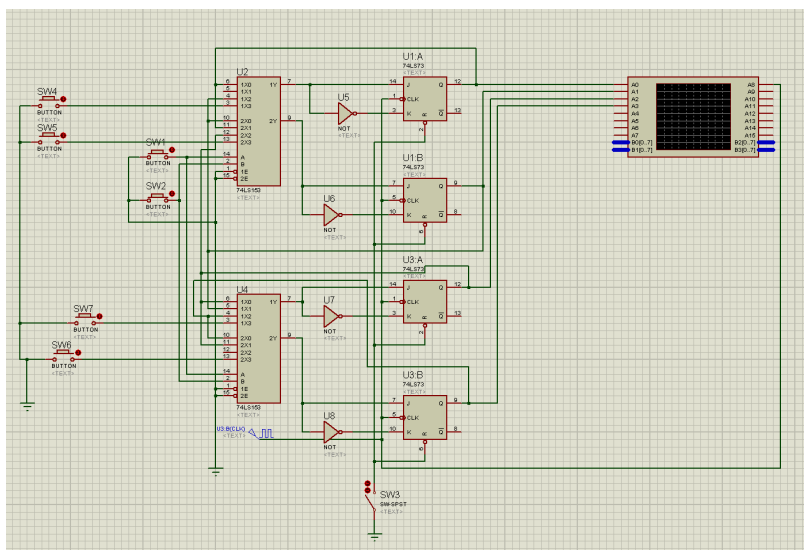


具体功能测试如下


1. 左移

 


2. 右移

 


3. 并行送数，图为1011

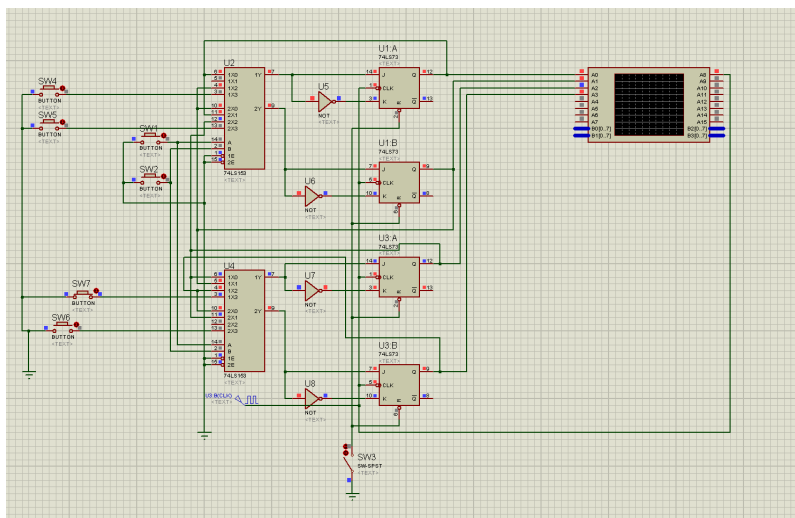

4. 保持，图为左移过程中出现0011后立即切换状态为保持

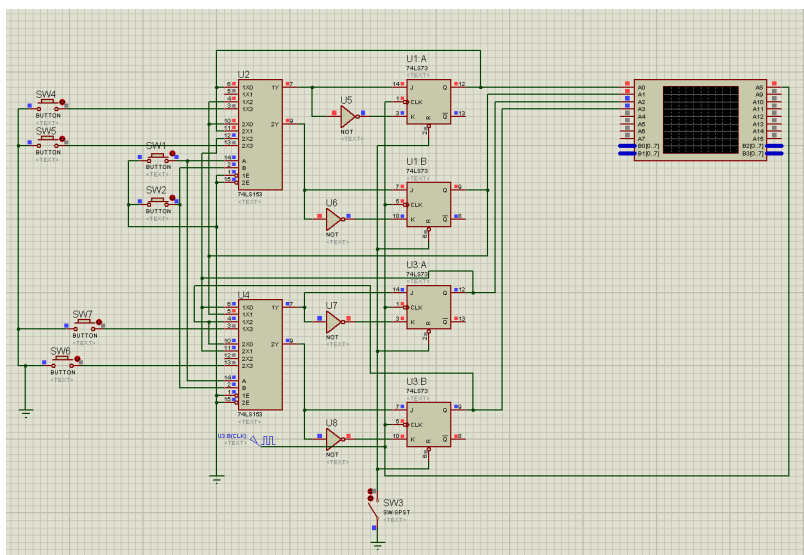

仅左移右移74LS194电路图如下

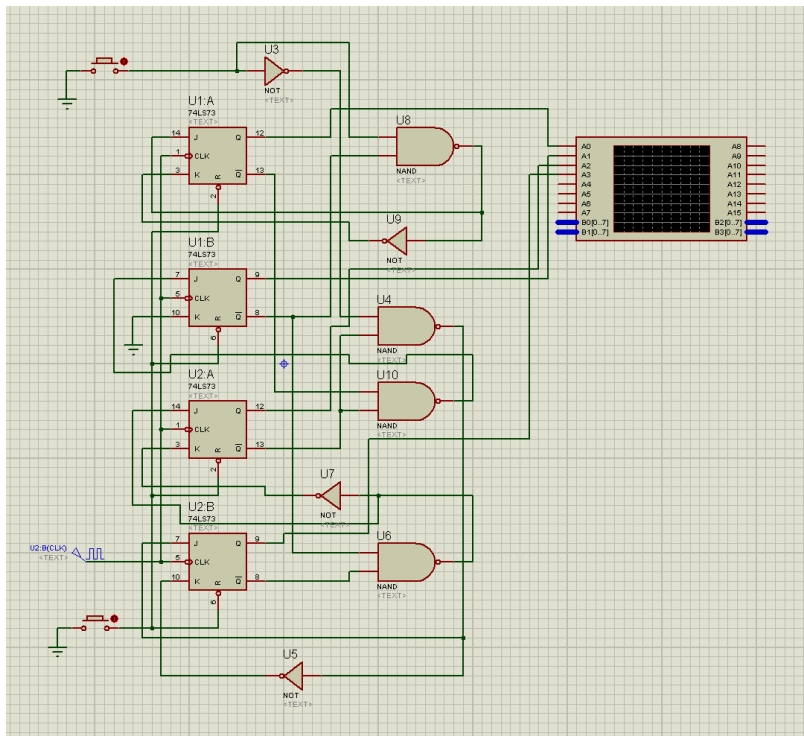


3.3.2 实验仪器及器件

1. 数字电路实验箱、示波器、导线若干
2. 74LS73*4

3.3.3 实验流程与结果分析

连线如Protues所示，结果如下图

 


4 内容四

4.1 实验目的

用JK触发器实现12进制同步计数器

4.2 实验原理

1. 状态转换图

 

2. 确定电路所需触发器数目

由于 $2^4 = 16 > 12$ ，故需要4个JK触发器

3. 次态卡诺图

Q ₃ Q ₂ \ Q ₁ Q ₀		00	01	11	10
		00	01	11	10
00		X	0010	0100	0011
01		0101	0110	1000	0111
11		0001	X	X	X
10		1001	1010	1100	1011

4. 触发器状态方程，由卡诺图可得

$$\begin{aligned}
 Q_0^{n+1} &= \overline{Q_0} \\
 Q_1^{n+1} &= Q_0 \overline{Q_1} + \overline{Q_0} Q_1 \\
 Q_2^{n+1} &= Q_0 Q_1 \overline{Q_2} + \overline{Q_1} Q_2 \overline{Q_3} + \overline{Q_0} Q_2 \overline{Q_3} \\
 Q_3^{n+1} &= \overline{Q_2} Q_3 + Q_0 Q_1 Q_2 \overline{Q_3}
 \end{aligned}$$

5. 触发器驱动方程，由

$$Q^{n+1} = J \overline{Q^n} + \overline{K} Q^n$$

将状态方程整理为上式形式，可得


$$\begin{aligned}
 J_0 &= 1 & K_0 &= 1 \\
 J_1 &= Q_0 & K_1 &= Q_0 \\
 J_2 &= Q_1 Q_0 & K_2 &= \overline{Q_3} \overline{Q_1} + \overline{Q_3} \overline{Q_0} = \overline{Q_3} + Q_1 Q_0 \\
 J_3 &= Q_2 Q_1 Q_0 & K_3 &= Q_2
 \end{aligned}$$

6. 检查自启动


当输入为1111和0000时，可自动跳转至0001；输入为1101时，跳转至0010；输入为1110时，跳转至0011

4.3 Protues仿真

电路图连接如下

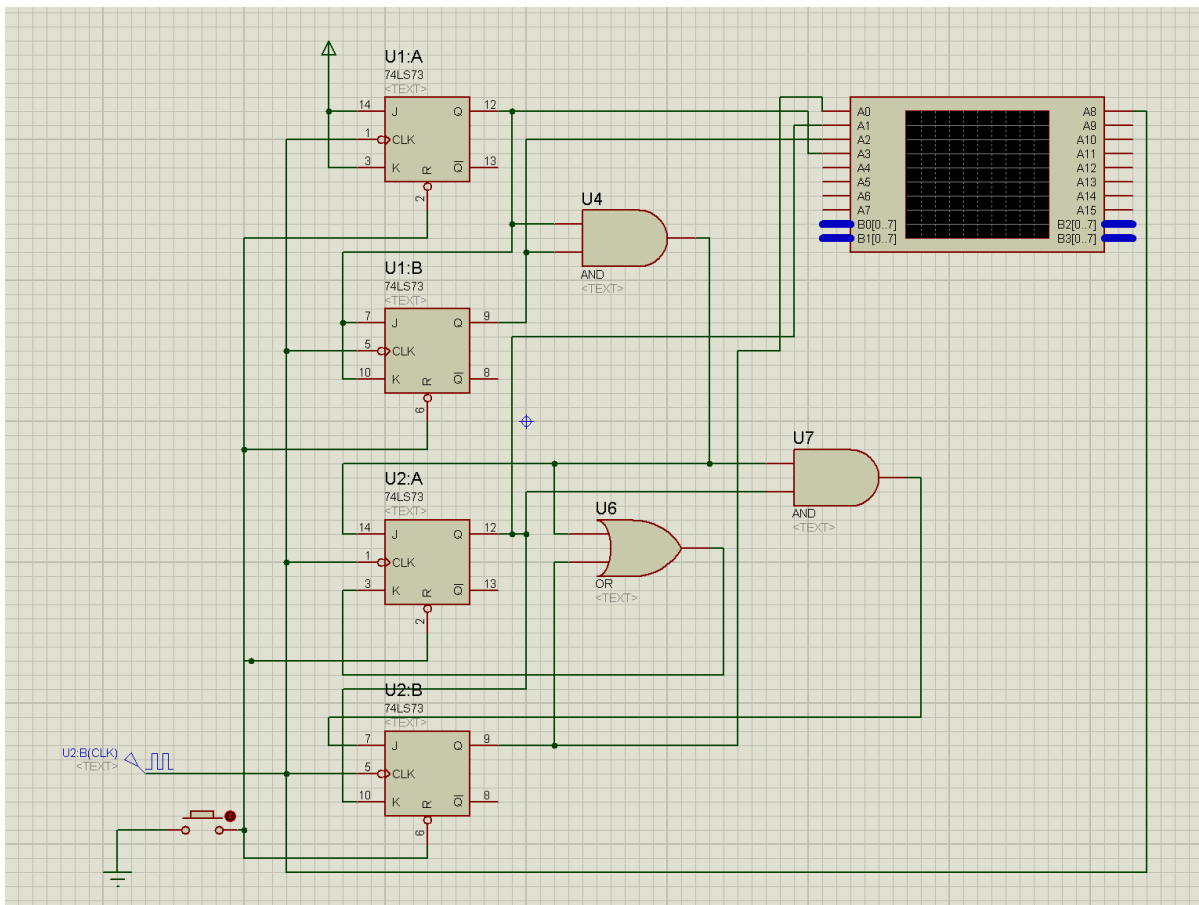

仿真结果如下

 

波形符合12进制转换

4.4 实验细节


4.4.1 实验仪器及器件

1. 数字电路实验箱、示波器、导线若干
2. 74LS73*4, 74LS00*2, 74LS08*2

4.4.2 实验流程与结果分析

如Protues电路图所示连线

将输出接01显示器，可见01显示器按照状态转换图顺序依次闪烁

 


5 内容五

5.1 实验目的

用Protues和Vivado分别实现一个有控制变量D的12进制计数器，并在七段数码管上显示计数结果

5.2 实验原理

1. 状态转移图

 

2. 次态卡诺图

Q ₃ Q ₂ \ Q ₁ Q ₀ D									
		000	001	011	010	110	111	101	100
00	X	X	11001	00100	01000	00101	00011	00110	
01	01010	00111	01001	01100	10000	01101	01011	01110	
11	00010	10111	X	X	X	X	X	X	
10	10010	01111	10001	10100	11000	10101	10011	10110	

3. 状态方程

$$Q_0^{n+1} = \overline{Q_0}$$

$$Q_1^{n+1} = \overline{Q_1} \overline{Q_0} D + \overline{Q_1} Q_0 \overline{D} + Q_1 Q_0 D + Q_1 \overline{Q_0} \overline{D} = (Q_0 \oplus D) \overline{Q_1} + \overline{Q_0} \oplus \overline{D} Q_1$$

$$\begin{aligned} Q_2^{n+1} &= \overline{Q_3} Q_2 \overline{Q_0} \overline{D} + \overline{Q_2} \overline{Q_1} \overline{Q_0} D + Q_2 \overline{Q_1} Q_0 + \overline{Q_3} \overline{Q_2} \overline{Q_1} D + Q_2 Q_1 D + \overline{Q_2} Q_1 Q_0 \overline{D} \\ &= (\overline{Q_1} \overline{Q_0} D + Q_1 Q_0 \overline{D} + \overline{Q_3} \overline{Q_1} D) \overline{Q_2} + (\overline{Q_3} \overline{Q_0} \overline{D} + \overline{Q_1} Q_0 + Q_1 D) Q_2 \end{aligned}$$

$$\begin{aligned} Q_3^{n+1} &= Q_3 Q_1 + \overline{Q_3} Q_2 Q_1 Q_0 \overline{D} + Q_3 Q_0 + Q_3 \overline{Q_2} \overline{Q_1} \overline{D} + Q_3 Q_2 D + \overline{Q_3} \overline{Q_2} \overline{Q_1} D \\ &= (Q_2 Q_1 Q_0 \overline{D} + \overline{Q_2} \overline{Q_1} D) \overline{Q_3} + (Q_1 + Q_0 + \overline{Q_2} \overline{Q_1} \overline{D} + Q_2 D) Q_3 \end{aligned}$$

4. 驱动方程

$$J_0 = 1$$

$$K_0 = 1$$

$$J_1 = Q_0 \oplus D$$

$$K_1 = Q_0 \oplus D$$

$$J_2 = \overline{Q_1} \overline{Q_0} D + Q_1 Q_0 \overline{D} + \overline{Q_3} \overline{Q_1} D$$


$$K_2 = \overline{Q_3} \overline{Q_0} \overline{D} + \overline{Q_1} Q_0 + Q_1 D$$

$$J_3 = Q_2 Q_1 Q_0 \overline{D} + \overline{Q_2} \overline{Q_1} D$$


$$K_3 = \overline{Q_1} + Q_0 + \overline{Q_2} \overline{Q_1} \overline{D} + Q_2 D$$

5.3 Protues仿真


电路图连接如下

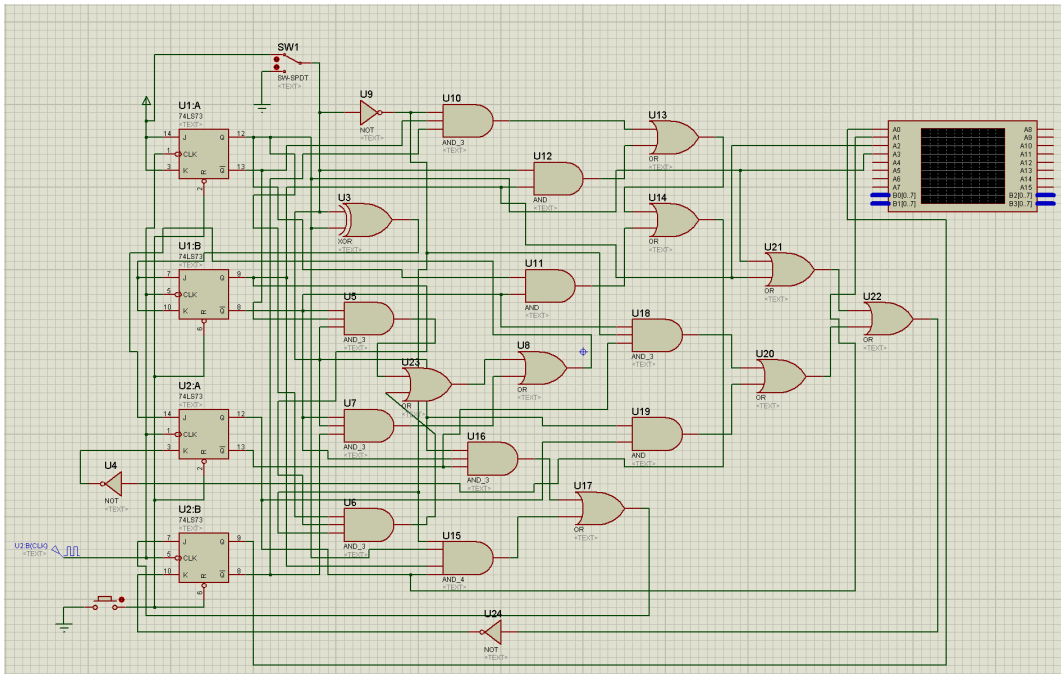

仿真结果如下，正向计数

 

逆向计数

 

波形符合12进制转换

5.4 Basys板电路实现

Verilog程序如下，12进制计数器部分，包括控制变量D的实现（变量名为fb）

```
module Counter(
    input clr, // clear, say reset
    input wire clk, // clock
    input wire fb, // add or minus
    output [6:0] seg,
    output [3:0] an
);

    reg [3:0] out;
    parameter MAX_COUNT = 12;

    // time counter
    localparam MAX_COUNT_TIME = 50_000_000; // 0.5s
    reg [25:0] count; // 26 bits to store count: 2^26 > 5*10^7
    always @ (posedge clk or posedge clr)
    begin
        if (clr == 1) // reset
            count <= 0;
        else if (count == MAX_COUNT_TIME - 1) // return 0
            count <= 0;
        else
            count <= count + 1;
    end

    // frequency divisor (flip-flop)
    reg clk_div;
    always @ (posedge clk, posedge clr)
    begin
        if (clr == 1)
            clk_div <= 0;
        else if (count == MAX_COUNT_TIME - 1) // reset
            clk_div <= ~clk_div;
        else // set
            clk_div <= clk_div;
    end

    // 12 system counter
    always @ (posedge clk_div or posedge clr)
    if (fb == 0)
```

```

begin
    if (clr == 1)
        out <= 0;
    if (out == MAX_COUNT)
        out <= 0;
    else
        out <= out + 1;
    end
else
begin
    if (clr == 1)
        out <= 0;
    if (out == 0)
        out <= 4'b1100;
    else
        out <= out - 1;
    end
end

display disp1 (.digit(out), .seven_seg(seg));

// only turn on the first seven segment display
assign an = 4'b1110;

endmodule

```

分频计数器与七段数码管连接部分

```

\scriptsize
module display (
    input [3:0] digit ,
    output reg [6:0] seven_seg
);

always @(digit)
    case(digit)
        1: seven_seg = 7'b100_1111;
        2: seven_seg = 7'b001_0010;
        3: seven_seg = 7'b000_0110;
        4: seven_seg = 7'b100_1100;
        5: seven_seg = 7'b010_0100;
        6: seven_seg = 7'b010_0000;
        7: seven_seg = 7'b000_1111;
        8: seven_seg = 7'b000_0000;
        9: seven_seg = 7'b000_0100;
        10: seven_seg = 7'b000_1000; // a
        11: seven_seg = 7'b110_0000; // b
        12: seven_seg = 7'b011_0001; // c
    endcase // clk

endmodule

```

限制文件如下

```

set_property PACKAGE_PIN W4 [get_ports {an[3]}]
set_property PACKAGE_PIN V4 [get_ports {an[2]}]
set_property PACKAGE_PIN U4 [get_ports {an[1]}]
set_property PACKAGE_PIN U2 [get_ports {an[0]}]
set_property PACKAGE_PIN W7 [get_ports {seg[6]}]
set_property PACKAGE_PIN W6 [get_ports {seg[5]}]
set_property PACKAGE_PIN U8 [get_ports {seg[4]}]
set_property PACKAGE_PIN V8 [get_ports {seg[3]}]
set_property PACKAGE_PIN U5 [get_ports {seg[2]}]
set_property PACKAGE_PIN V5 [get_ports {seg[1]}]
set_property PACKAGE_PIN U7 [get_ports {seg[0]}]

set_property PACKAGE_PIN W5 [get_ports clk]
set_property IOSTANDARD LVCMOS33 [get_ports {an[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {an[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {an[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {an[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[0]}]

```


```

set_property IOSTANDARD LVCOS33 [get_ports {seg[2]}]
set_property IOSTANDARD LVCOS33 [get_ports {seg[1]}]
set_property IOSTANDARD LVCOS33 [get_ports {seg[0]}]
set_property IOSTANDARD LVCOS33 [get_ports clk]

set_property PACKAGE_PIN V17 [get_ports clr]
set_property PACKAGE_PIN R2 [get_ports fb]
set_property IOSTANDARD LVCOS33 [get_ports clr]
set_property IOSTANDARD LVCOS33 [get_ports fb]

```

最终结果图如下

 

通过调整最左下角的拨码开关，可实现任意时刻计数器的正向计数和反向计数

6 心得体会

1. 学会了移位寄存器及JK触发器的使用及其功能
2. 明白同步异步时序电路如何进行设计
3. 更好地学会用Verilog进行电路设计分析，并成功上板实现